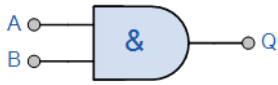



Analog and Digital Electronics


Prof. Kalpesh Dudani
Electrical Engineering Department
L. E. College, Morbi


Logic Gates


Symbol	Truth Table		
AND	B	A	Q
	0	0	0
	0	1	0
	1	0	0
	1	1	1
Boolean Expression $Q = A \cdot B$	Read as A AND B gives Q		

Symbol	Truth Table		
NAND	B	A	Q
	0	0	1
	0	1	1
	1	0	1
	1	1	0
Boolean Expression $Q = \overline{A \cdot B}$	Read as A AND B gives NOT Q		

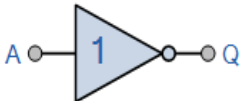Symbol	Truth Table	
NOT	A	Q
	0	1
	1	0
Boolean Expression $Q = \text{not } A \text{ or } \overline{A}$	Read as inverse of A gives Q	

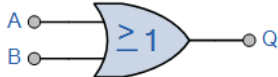
Symbol	Truth Table		
OR	B	A	Q
	0	0	0
	0	1	1
	1	0	1
	1	1	1
Boolean Expression $Q = A + B$	Read as A OR B gives Q		

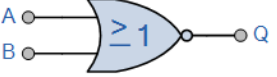Symbol	Truth Table		
NOR	B	A	Q
	0	0	1
	0	1	0
	1	0	0
	1	1	0
Boolean Expression $Q = \overline{A + B}$	Read as A OR B gives NOT Q		

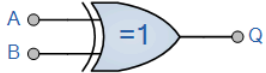Symbol	Truth Table		
Ex-OR	B	A	Q
	0	0	0
	0	1	1
	1	0	1
	1	1	0
Boolean Expression $Q = A \oplus B$	Read as A OR B but not BOTH gives Q (odd)		

Boolean Algebra

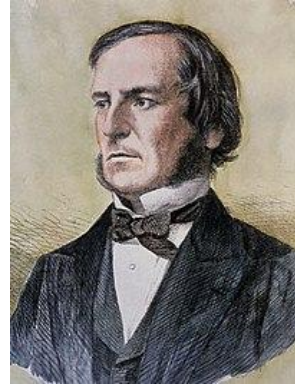Boolean algebra was invented by George Boole in 1854



- Boolean Algebra is used to analyze and simplify the digital (logic) circuits.
 - It uses only the binary numbers i.e. 0 and 1.
 - It is also called as Binary Algebra or logical Algebra.
 - This can help lower the cost and raise the speed and efficiency of digital circuits
-
- Digital circuits are made up of **logic gates**.
 - Logic gates are a fundamental digital component that perform simple logical calculations
 - Multiple logic gates can be connected with wires, forming a complex digital circuit.
 - Outputs of logic gates can be connected to the inputs of other logic gates.
 - When multiple logic gates work together, they can perform complex mathematical calculations, as well as remember data.

“Set of rules used to simplify the given logic expression without changing its functionality”

Boolean Algebra

Laws of Boolean Algebra:

AND law:

$$A.0 = 0$$

$$A.1 = A$$

$$A.A = A$$

$$A.A' = 0$$

OR law:

$$A + 0 = A$$

$$A + 1 = 1$$

$$A + A = A$$

$$A + A' = 1$$

Complement law:

$$(A')' = A$$

Commutative law:

$$A.B = B.A$$

$$A + B = B + A$$

Associative law:

$$(A.B).C = A.(B.C)$$

$$(A + B) + C = A + (B + C)$$

Distributive law:

$$A.(B + C) = A.B + A.C$$

$$A + B.C = (A + B).(A + C)$$

De Morgan's rule:

$$(A + B)' = A' . B'$$

$$(A . B)' = A' + B'$$

Other imp. rules:

$$A + AB = A$$

$$A + A'B = A + B$$

$$A' + AB = A' + B$$

$$A' + AB' = A' + B'$$

Boolean Algebra

Solve

$$AB + AB'$$

$$A \cdot (B + B')$$

$$A \cdot 1$$

$$A$$

$$AB + AB'C + AB'C'$$

$$A(B + B'C + B'C')$$

$$A(B + C + B'C')$$

$$A(B + C + C')$$

$$A(B + 1)$$

$$A(1)$$

$$A$$

$$(A')' = A$$

$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$

$$A \cdot A = A$$

$$A \cdot A' = 0$$

$$A + 0 = A$$

$$A + 1 = 1$$

$$A + A = A$$

$$A + A' = 1$$

$$A \cdot (B + C) = A \cdot B + A \cdot C$$

$$A + B \cdot C = (A + B) \cdot (A + C)$$

$$A + A' \cdot B = A + B$$

$$A' + AB = A' + B$$

$$(A + B)' = A' \cdot B'$$

$$(A \cdot B)' = A' + B'$$

Boolean Algebra

Solve

$$(A+B+C)(A+B'+C)(A+B+C')$$

$$(X+C)(A+B'+C)(X+C')$$

$$(X+C)(X+C')(A+B'+C)$$

$$(X+CC')(A+B'+C)$$

$$(X+0)(A+B'+C)$$

$$X(A+B'+C)$$

$$(A+B)(A+B'+C)$$

$$A+B(B'+C)$$

$$A+BB'+BC$$

$$A+BC$$

$$(A')' = A$$

$$A.0 = 0$$

$$A.1 = A$$

$$A.A = A$$

$$A.A' = 0$$

$$A+0 = A$$

$$A+1 = 1$$

$$A+A = A$$

$$A+A' = 1$$

$$A.(B+C) = A.B + A.C$$

$$A+B.C = (A+B).(A+C)$$

$$A+A'B = A+B$$

$$A'+AB = A'+B$$

$$(A+B)' = A' \cdot B'$$

$$(A \cdot B)' = A' + B'$$

Boolean Algebra

Solve

$$(A+B)(A+B')(A'+B)(A'+B')$$

$$(A+BB')(A'+BB')$$

$$(A+0)(A'+0)$$

$$AA'$$

$$0$$

$$(A')' = A$$

$$A.0 = 0$$

$$A.1 = A$$

$$A.A = A$$

$$A.A' = 0$$

$$A+0 = A$$

$$A+1 = 1$$

$$A+A = A$$

$$A+A' = 1$$

$$A.(B+C) = A.B + A.C$$

$$A+B.C = (A+B).(A+C)$$

$$A+A'B = A+B$$

$$A'+AB = A'+B$$

$$(A+B)' = A' \cdot B'$$

$$(A \cdot B)' = A' + B'$$

Boolean Algebra

Redundancy Theorem

- Three variables
 - Each variable represented twice
 - One variable is complimented
- Take complemented variable

$$AB + A'C + BC$$

$$AB + A'C$$

$$AB + A'C + BC$$

$$AB + A'C + BC(A + A')$$

$$AB + A'C + ABC + A'BC$$

$$AB(1 + C) + A'C(1 + B)$$

$$AB(1) + A'C(1)$$

$$AB + A'C$$

Boolean Algebra

Redundancy Theorem

- Three variables
 - Each variable represented twice
 - One variable is complimented
- Take complemented variable

$$AB + BC' + AC$$

$$BC' + AC$$

$$(A + B)(A' + C)(B + C)$$

$$(A + B)(A' + C)$$

$$A'B' + AC' + B'C'$$

$$A'B' + AC'$$

Sum of Product (SOP)

SOP → when output is “1”

Standard or
canonical
SOP form

	A	B	C	Y
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	0
m_4	1	0	0	1
m_5	1	0	1	1
m_6	1	1	0	1
m_7	1	1	1	1

$$Y = A'BC' + AB'C' + AB'C + ABC' + ABC$$

$$Y = A'BC' + AB'C' + AB'C + ABC' + ABC$$

$$Y = A'BC' + AB'(C' + C) + AB(C' + C)$$

$$Y = A'BC' + AB' + AB$$

$$Y = A'BC' + A(B' + B)$$

$$Y = A'BC' + A$$

$$Y = A + BC'$$

Minimal
SOP form

$$F(A, B, C) = m_2 + m_4 + m_5 + m_6 + m_7 = \sum m(2, 4, 5, 6, 7)$$

Sum of Product (SOP)

A	B	Y
0	0	0
0	1	1
1	0	0
1	1	1

For the given Truth Table, Minimize the SOP expression

$$Y = A' \cdot B + A \cdot B$$

$$Y = B \cdot (A' + A)$$

$$Y = B \cdot 1$$

$$Y = B$$

	A	B	Y
m_0	0	0	1
m_1	0	1	0
m_2	1	0	1
m_3	1	1	1

Simplify the expression for $Y(A,B)=\Sigma m(0,2,3)$

$$Y = m_0 + m_2 + m_3$$

$$Y = A' B' + A B' + A B$$

$$Y = B'(A' + A) + A B$$

$$Y = B' + A B$$

$$Y = B' + A$$

Sum of Product (SOP)

A	B	Y
0	0	1
0	1	1
1	0	0
1	1	1

For the given Truth Table, Minimize the SOP expression

$$Y = A \cdot B + A' \cdot B + A \cdot B$$

$$Y = A \cdot B + B \cdot (A' + A)$$

$$Y = A \cdot B + B$$

$$Y = A \cdot B$$

	A	B	Y
m_0	0	0	0
m_1	0	1	1
m_2	1	0	1
m_3	1	1	1

Simplify the expression for $Y(A,B)=\Sigma m(1,2,3)$

$$Y = m_1 + m_2 + m_3$$

$$Y = A' \cdot B + A \cdot B' + A \cdot B$$

$$Y = A' \cdot B + A(B' + B)$$

$$Y = A' \cdot B + A$$

$$Y = A + B$$

Product of Sum (POS)

POS → when output is “0”

Standard or
canonical
POS form

	A	B	C	Y
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	0
m_4	1	0	0	1
m_5	1	0	1	1
m_6	1	1	0	1
m_7	1	1	1	1

$$Y = (A + B + C) \cdot (A + B + C') \cdot (A + B' + C')$$

$$Y = (A + B + C) \cdot (A + B + C') \cdot (A + B' + C')$$

$$Y = A + B(C \cdot C') \cdot (A + B' + C')$$

$$Y = (A + B) \cdot (A + B' + C')$$

$$Y = A + B \cdot (B' + C')$$

$$Y = A + BC'$$

Minimal
POS form

Sum of Product (POS)

A	B	Y
0	0	1
0	1	0
1	0	1
1	1	0

For the given Truth Table, Minimize the POS expression

$$Y = (A + B').(A' + B')$$

$$Y = B' + A.A'$$

$$Y = B'$$

	A	B	Y
M_0	0	0	0
M_1	0	1	1
M_2	1	0	0
M_3	1	1	1

Simplify the expression for $Y(A,B)=\Pi m(0,2)$

$$Y = M_0 + M_2$$

$$Y = (A + B).(A' + B)$$

$$Y = B + A.A'$$

$$Y = B$$

SOP & POS

	A	B	C	F
m_0	0	0	0	1
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	1
m_4	1	0	0	0
m_5	1	0	1	0
m_6	1	1	0	1
m_7	1	1	1	1

$$Y(A, B, C) = \sum m(0, 2, 3, 6, 7)$$

$$Y = A'B'C' + A'BC' + A'BC + ABC' + ABC$$

$$Y = A'B'C' + A'B + AB$$

$$Y = A'B'C' + B$$

$$Y = B + A'C'$$

$$Y(A, B, C) = \prod M(1, 4, 5)$$

$$Y = (A + B + C')(A' + B + C)(A' + B + C')$$

$$Y = (A + B + C')(A' + B)$$

$$Y = (B + A + C')(B + A')$$

$$Y = B + (A + C').A'$$

$$Y = B + A'C'$$

SOP: Minimal to Canonical form

$$Y = A + B'C$$

Step 1: Check number of variables (A, B, C)

Step 2: Check availability of variables in minimal (m_1, m_2)

m_1	m_2
A: ✓	A: x
B: x	B: ✓
C: x	C: ✓

Step 3: Write down missing variable $\rightarrow 1$ as $(x+x')$

$$Y = A \cdot 1 \cdot 1 + B' \cdot C \cdot 1$$

$$Y = A \cdot (B + B') \cdot (C + C') + B' \cdot C \cdot (A + A')$$

$$Y = (AB + AB') \cdot (C + C') + B' \cdot C \cdot A + B' \cdot C \cdot A'$$

$$Y = ABC + ABC' + AB'C + AB'C' + AB'C + A'B'C$$

$$Y = ABC + ABC' + AB'C + AB'C' + A'B'C$$

POS: Minimal to Canonical form

$$Y = (A + B + C') \cdot (A' + C)$$

Step 1: Check number of variables (A, B, C)

Step 2: Check availability of variables in minimal (m_1 , m_2)

m_1	m_2
A: ✓	A: ✓
B: ✓	B: x
C: ✓	C: ✓

Step 2: Write down missing variable $\rightarrow 0$ as (x.x')

$$Y = (A + B + C') \cdot (A' + C)$$

$$Y = (A + B + C') \cdot (A' + C + 0)$$

$$Y = (A + B + C') \cdot (A' + C + B \cdot B')$$

$$Y = (A + B + C') \cdot (A' + C + B) \cdot (A' + C + B')$$

Karnaugh Map (K-Map)

Maurice Karnaugh, developed the K-Map at Bell Labs in 1953 while designing digital logic based telephone switching circuits

- Reduce logic function more quickly and easily than Boolean algebra

Karnaugh Map (K-Map)

Find minimal form using SOP $A + BC'$

A	B	C	Y	
0	0	0	0	m_0
0	0	1	0	m_1
0	1	0	1	m_2
0	1	1	0	m_3
1	0	0	1	m_4
1	0	1	1	m_5
1	1	0	1	m_6
1	1	1	1	m_7

		BC			
		00	01	11	10
A	0				1
	1	1	1	1	1

Pairing: 1, 2, 4, 8


$$Y = I + II \text{ (Implicants)}$$

$$Y = A + BC'$$

Karnaugh Map (K-Map)

$$f(A, B, C) = \sum m(1, 3, 5, 7)$$

A	B	C	Y	
0	0	0	0	m_0
0	0	1	1	m_1
0	1	0	0	m_2
0	1	1	1	m_3
1	0	0	0	m_4
1	0	1	1	m_5
1	1	0	0	m_6
1	1	1	1	m_7

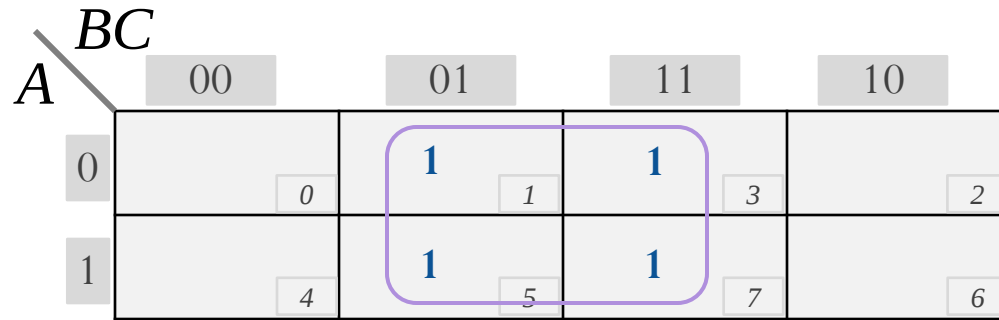

Pairing: 1, 2, 4, 8

$Y = I$ (Implicants)

$Y = C$

Karnaugh Map (K-Map)

$$f(A, B, C) = \sum m(0, 1, 2, 4, 7)$$

		<i>BC</i>			
		00	01	11	10
<i>A</i>	0	1	1		1
	1	1		1	

Pairing: 1, 2, 4, 8

$$Y = I + II + III + IV$$

$$Y = B'C' + A'B' + ABC + A'C'$$

Karnaugh Map (K-Map)

$$f(A, B, C) = \sum m(1, 3, 6, 7)$$

$A \backslash BC$					
		00	01	11	10
0			1	1	
1				1	1

Pairing: 1, 2, 4, 8

$$Y = I + II$$

$$Y = A'C + AB$$

Karnaugh Map (K-Map)

$$f(A, B, C) = \sum m(1, 3, 6, 7)$$

BC A					
		00	01	11	10
0			1	1	
1				1	1

Pairing: 1, 2, 4, 8

$$Y = I + II$$

$$Y = A'C + AB + BC$$

$$Y = A'C + AB \quad (\because \text{Redundancy Theorem})$$

Karnaugh Map (K-Map)

$$f(A, B, C) = \sum m(0, 1, 5, 6, 7)$$

		<i>BC</i>			
		00	01	11	10
<i>A</i>	0	1	1		
	1		1	1	1

Pairing: 1, 2, 4, 8

$$Y = I + II + III_A$$

$$Y = AB + AB' + AC$$

$$Y = I + II + III_B$$


$$Y = AB + AB' + B'C$$

Karnaugh Map (K-Map) - Implicants

Implicants: Group of 1's

Prime Implicants: Largest possible group of 1's

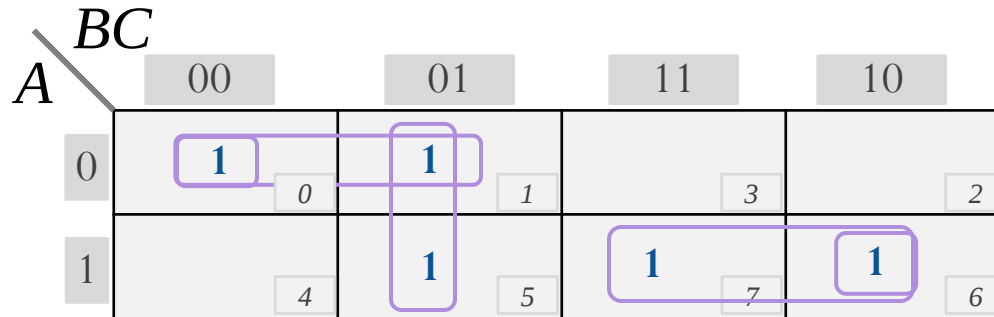Essential Prime Implicants: Single 1 which can not be combined in any other way



Karnaugh Map (K-Map) – 4 variable

$$f(A, B, C, D) = \sum m(0, 2, 3, 7, 11, 13, 14, 15)$$


$AB \backslash CD$					
		00	01	11	10
00	1	0	1	3	2
01	4	5	7	6	
11	12	13	15	14	
10	8	9	11	10	

$$Y = I + II + III + IV$$

$$Y = CD + A'B'D' + ABD + ABC$$

Karnaugh Map (K-Map)
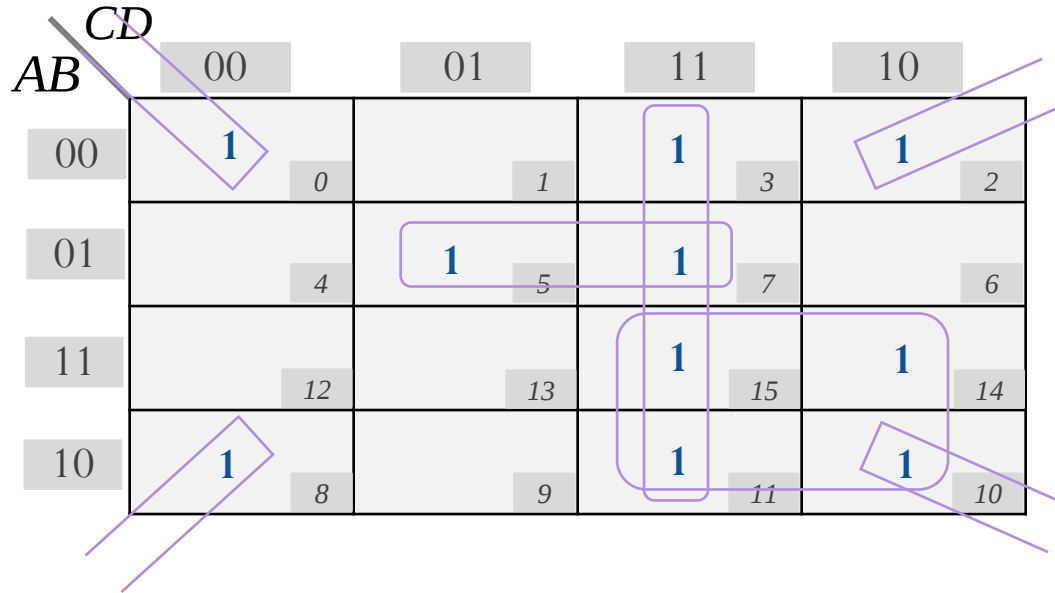
$$f(A, B, C, D) = \sum m(0, 2, 3, 5, 7, 8, 10, 11, 14, 15)$$



$$Y = I + II + III + IV$$

$$Y = CD + B'D' + AC + A'BD$$

Karnaugh Map (K-Map)

$$f(A, B, C, D) = \sum m(1, 5, 7, 9, 11, 13, 15)$$

$AB \backslash CD$					
		00	01	11	10
00		0	1	3	2
01		4	5	7	6
11		12	13	15	14
10		8	9	11	10

$$Y = I + II + III$$

$$Y = C'D + AD + BD$$

Karnaugh Map (K-Map) – Using Maxterm

		<i>BC</i>			
		00	01	11	10
<i>A</i>	0	1 <i>m</i> ₀	1 <i>m</i> ₁	0 <i>m</i> ₃	0 <i>m</i> ₂
	1	1 <i>m</i> ₄	1 <i>m</i> ₅	1 <i>m</i> ₇	1 <i>m</i> ₆

$$Y = I + II$$

$$Y = A + B'$$

$$Y = I$$

$$Y = A + B'$$

OR

$$Y = I$$

$$Y' = (A'B)'$$

$$Y' = A + B'$$

Karnaugh Map (K-Map) – Don't care condition

$$f(A, B, C) = \sum m(2, 3, 4, 5) + \sum d(6, 7)$$

BC		00	01	11	10
A	0			1	1
	1	1	1	1	1

Note: The K-map above represents the function f(A,B,C) = Σm(2,3,4,5) + Σd(6,7). The cells m3, m2, m4, m5, m6, and m7 are marked with 1. The cells m6 and m7 are circled in purple, indicating they are don't care conditions.

In Minterm(SOP) replace Don't care by 1

In Maxterm(POS) replace Don't care by 0

$$Y = I + II$$

$$Y = A + B$$

OR gate



$$Y = I + II$$

$$Y = A'B + AB'$$

AND, OR, AND gate


5 variable Karnaugh Map (K-Map)

A	B	C	D	E
0	0	0	0	0
0	0	0	0	1
0	0	0	1	0
0	0	0	1	1
0	0	1	0	0
0	0	1	0	1
0	0	1	1	0
0	0	1	1	1
0	1	0	0	0
.	1	0	0	1
.	1	0	1	0
.	1	0	1	1
.	1	1	0	0
.	1	1	0	1
0 ₁₆	1	1	1	0
	1	1	1	1

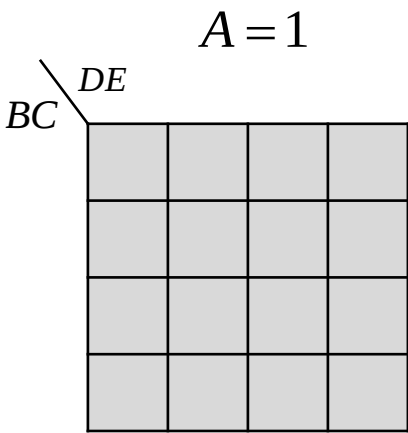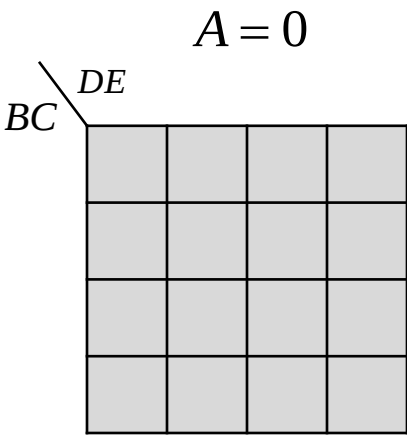


A	B	C	D	E
1	0	0	0	0
1	0	0	0	1
1	0	0	1	0
1	0	0	1	1
1	0	1	0	0
1	0	1	0	1
1	0	1	1	0
1	0	1	1	1
1	1	0	0	0
.	1	0	0	1
.	1	0	1	0
.	1	0	1	1
.	1	1	0	0
.	1	1	0	1
.	1	1	1	0
1 ₁₆	1	1	1	1

5 variable Karnaugh Map (K-Map)

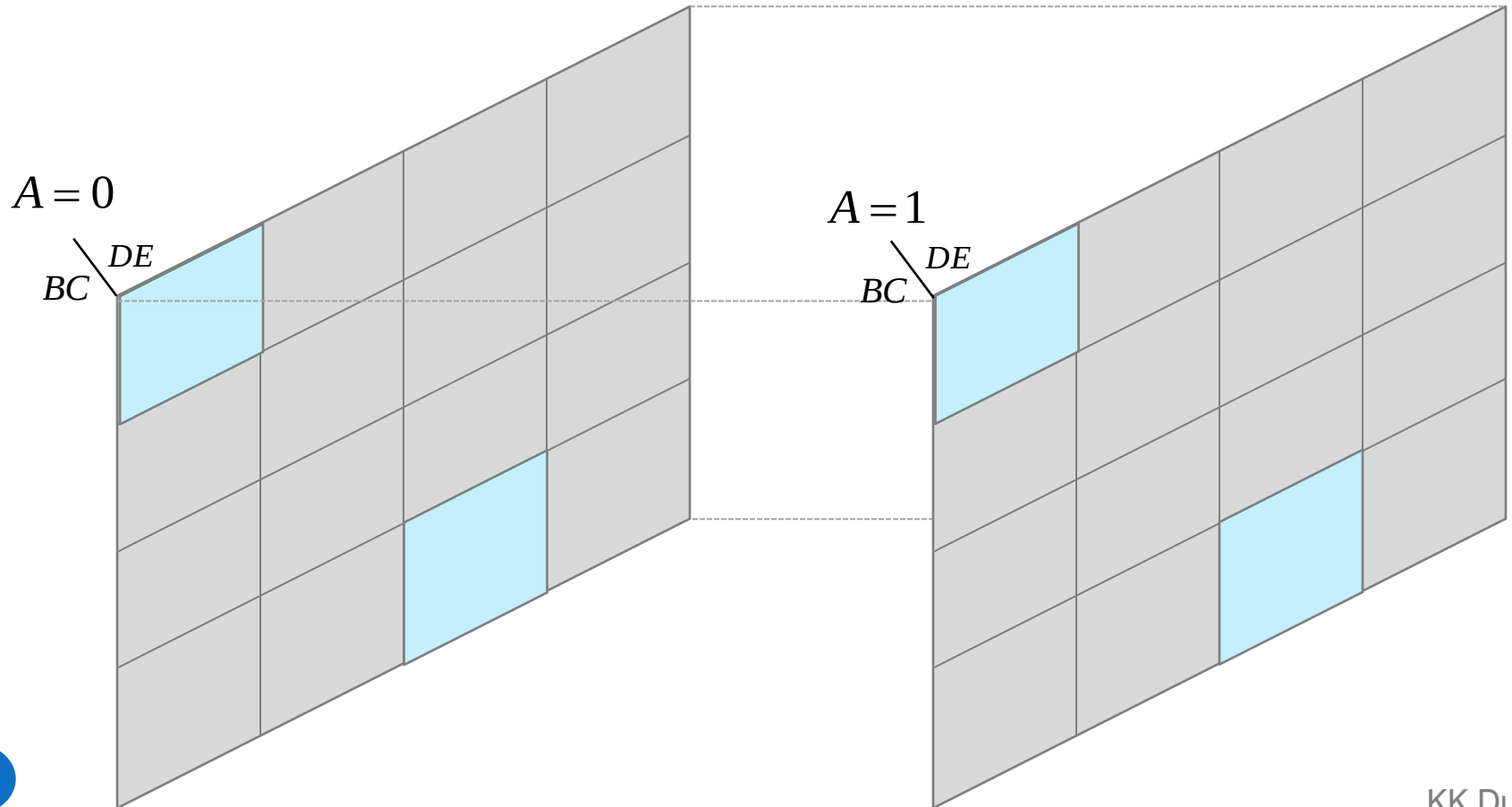

5 variable Karnaugh Map (K-Map)

A = 0

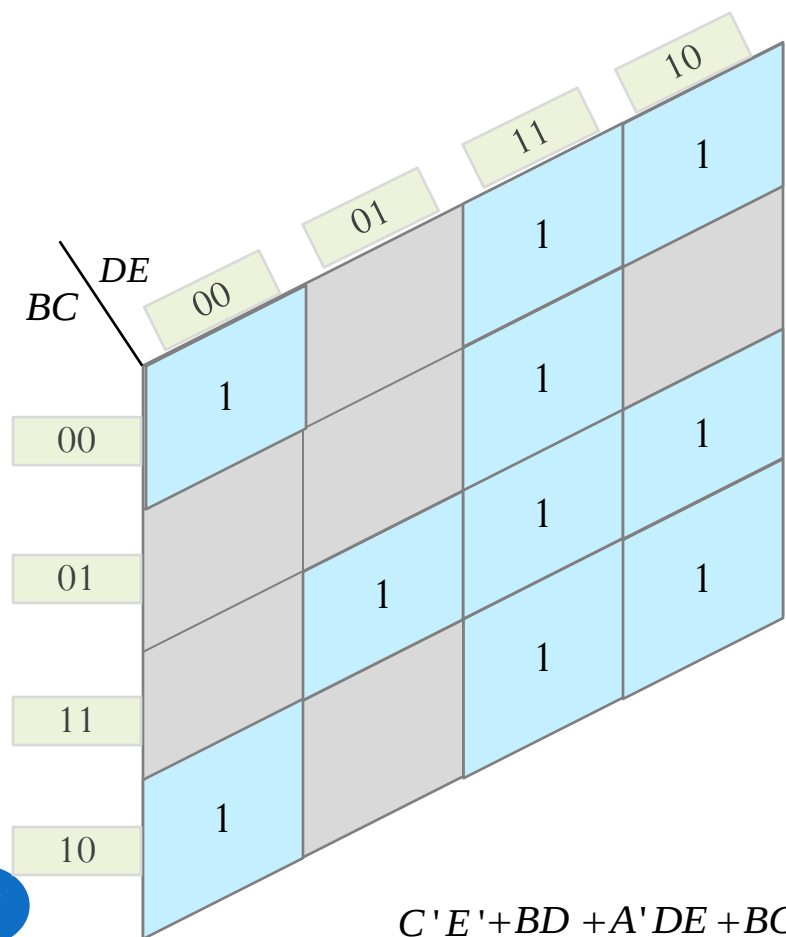

$C'E' + BD + A'DE + BCE$

A = 1

